 


Summary of previous lecture

- number representation: usually two's complement, but other representations possible
- choice depends on hardware size, performance, development time, availability of design tools etc
- ALU:



- develop efficient, regular bit-level design from obvious word-level design
- size/performance trade-offs in different architectures e.g. ripple-carry adder versus carry-select adder

Multiply and divide

(3rd Ed: p.250-274, 4th Ed: p.230-242, 5th Ed: p.183-196)

- implementing multiplication using ALU
- Booth's multiplication algorithm
- implementing division using ALU
- related MIPS instructions
 - mult, multu, div, divu, mfhi, mflo, sll, srl, sra

Multiply: example


- multiplicand \times multiplier = product

$$2 \quad \times \quad 11 \quad = \quad 22$$

- idea: sum of multiplicand shifted successively by 1 bit relative to multiplier; CSAA


- | | | | |
|----------------------------|---------|---|--|
| | 0010 | mc | |
| × | 1011 | mp | |
| <hr style="width: 100%;"/> | | | |
| | ...0010 | ← mc shifted 0 bit \times bit 0 of mp | |
| | ..0010. | ← " " 1 " \times " 1 " | |
| + | 0010... | ← " " 3 " \times " 3 " | |
| <hr style="width: 100%;"/> | | | |
| | 0010110 | | |

Multiplication hardware: first version

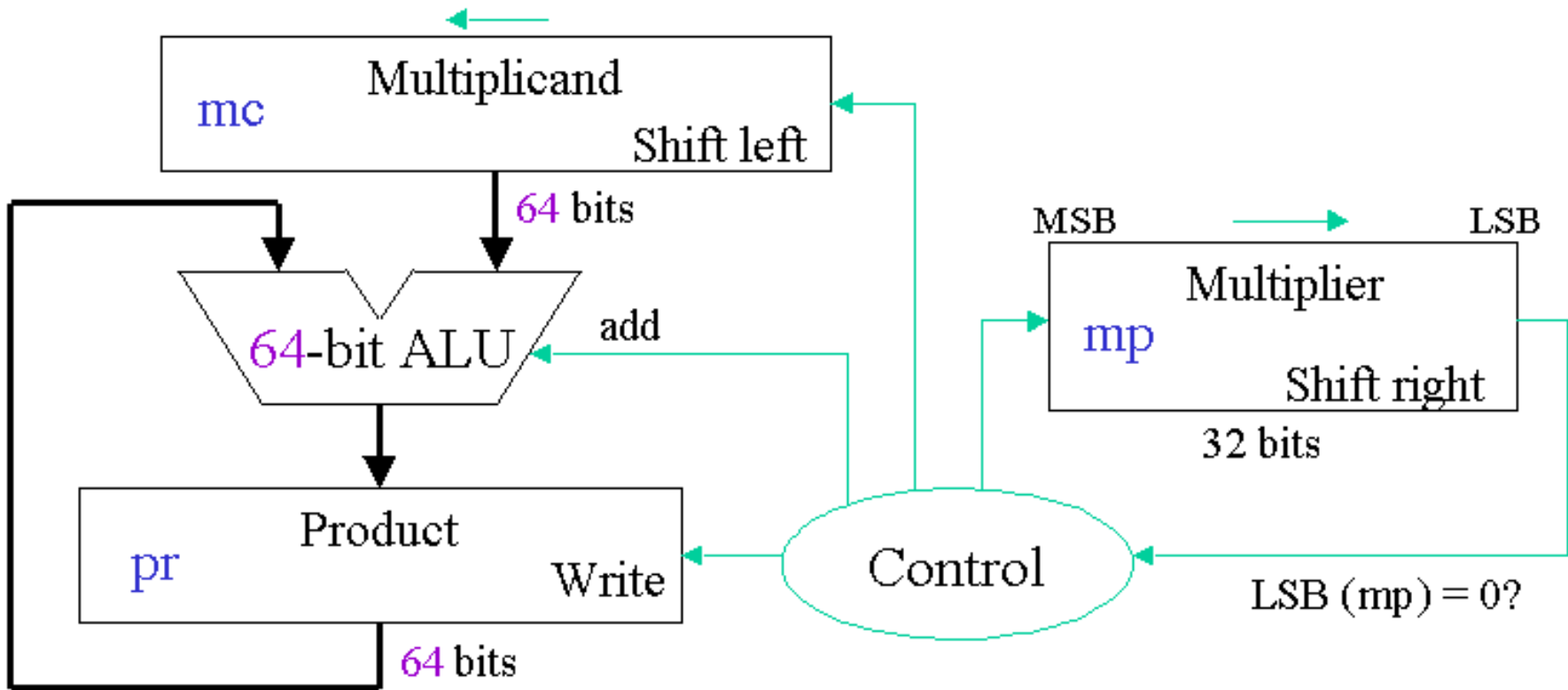

The multiplicand register, ALU, and Product register are all 64 bits wide, with only the Multiplier register containing 32 bits. The 32-bit multiplicand starts in the right half of the Multiplicand register, and is shifted left 1 bit on each step. The multiplier is shifted in the opposite direction at each step. The algorithm starts with the product initialised to 0. Control decides when to shift the Multiplicand and Multiplier registers and when to write new values into the Product register.


$$pr = mp \times mc$$

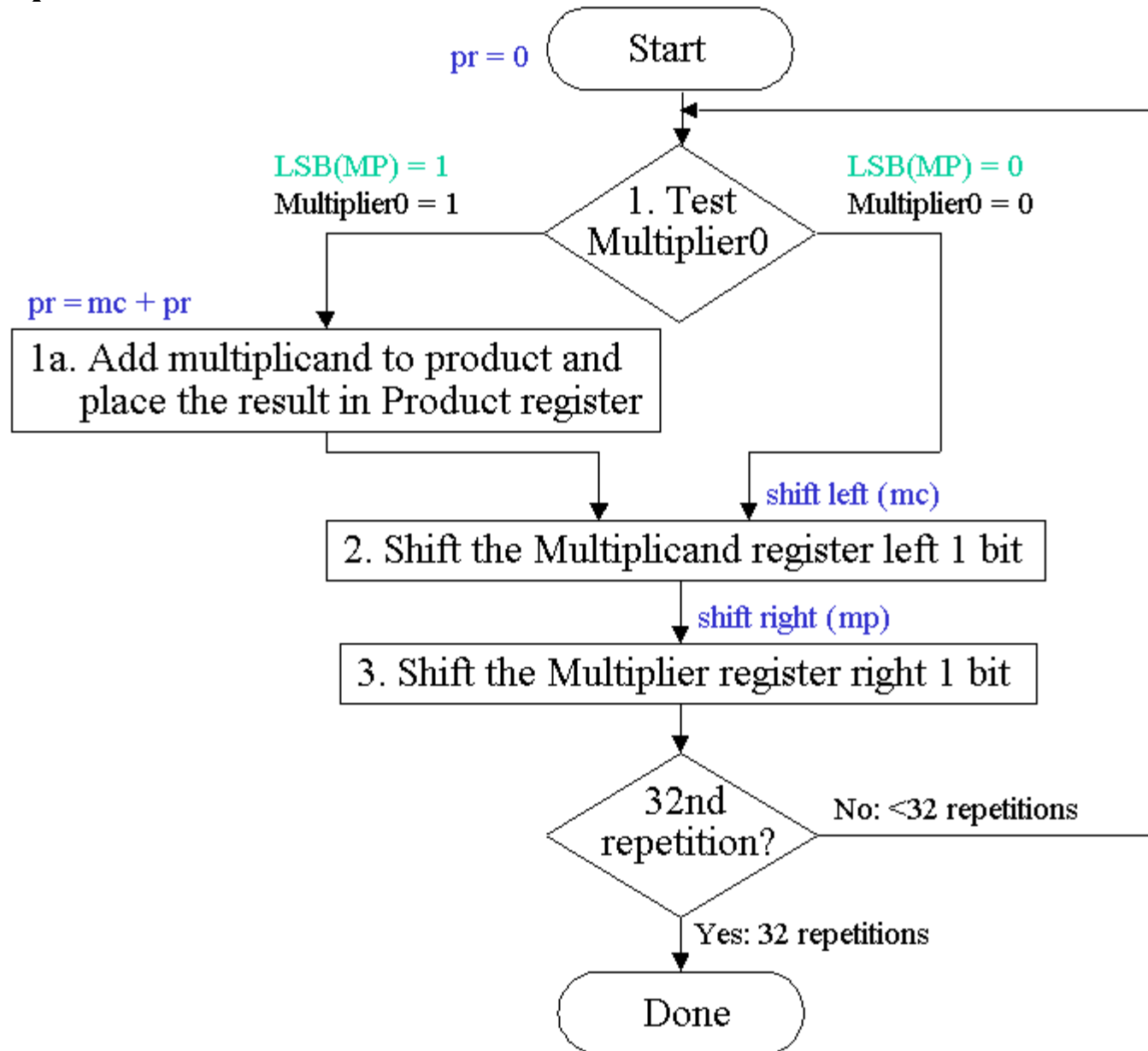

Multiply example using first algorithm

Iteration	Step	Multiplier	Multiplicand	Product
0	Initial Values	001 1	0000 0010	0000 0000
1	1a: 1 => Prod=Prod+Mcand	0011	0000 0010	0000 0010
	2: Shift left Multiplicand	0011	0000 0100	0000 0010
	3: Shift right Multiplier	000 1	0000 0100	0000 0010
2	1a: 1 => Prod=Prod+Mcand	0001	0000 0100	0000 0110
	2: Shift left Multiplicand	0001	0000 1000	0000 0110
	3: Shift right Multiplier	000 0	0000 1000	0000 0110
3	1: 0 => no operation	0000	0000 1000	0000 0110
	2: Shift left Multiplicand	0000	0001 0000	0000 0110
	3: Shift right Multiplier	000 0	0001 0000	0000 0110
4	1: 0 => no operation	0000	0001 0000	0000 0110
	2: Shift left Multiplicand	0000	0010 0000	0000 0110
	3: Shift right Multiplier	0000	0010 0000	0000 0110


Multiplication hardware: second version

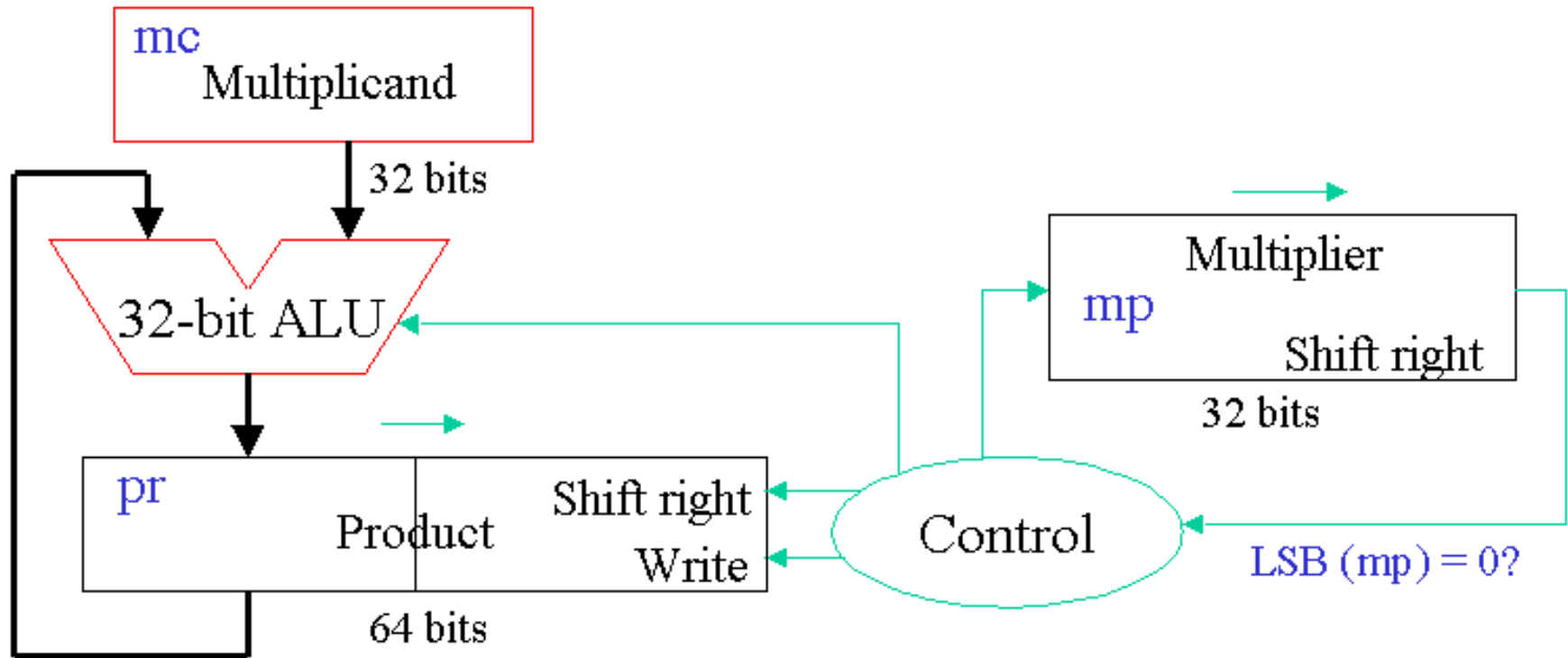

The Multiplicand register, ALU, and Multiplier register are all 32 bits wide, with only the Product register left as 64 bits. Now the product is shifted right.

$$pr = mp \times mc$$


LH: left Half

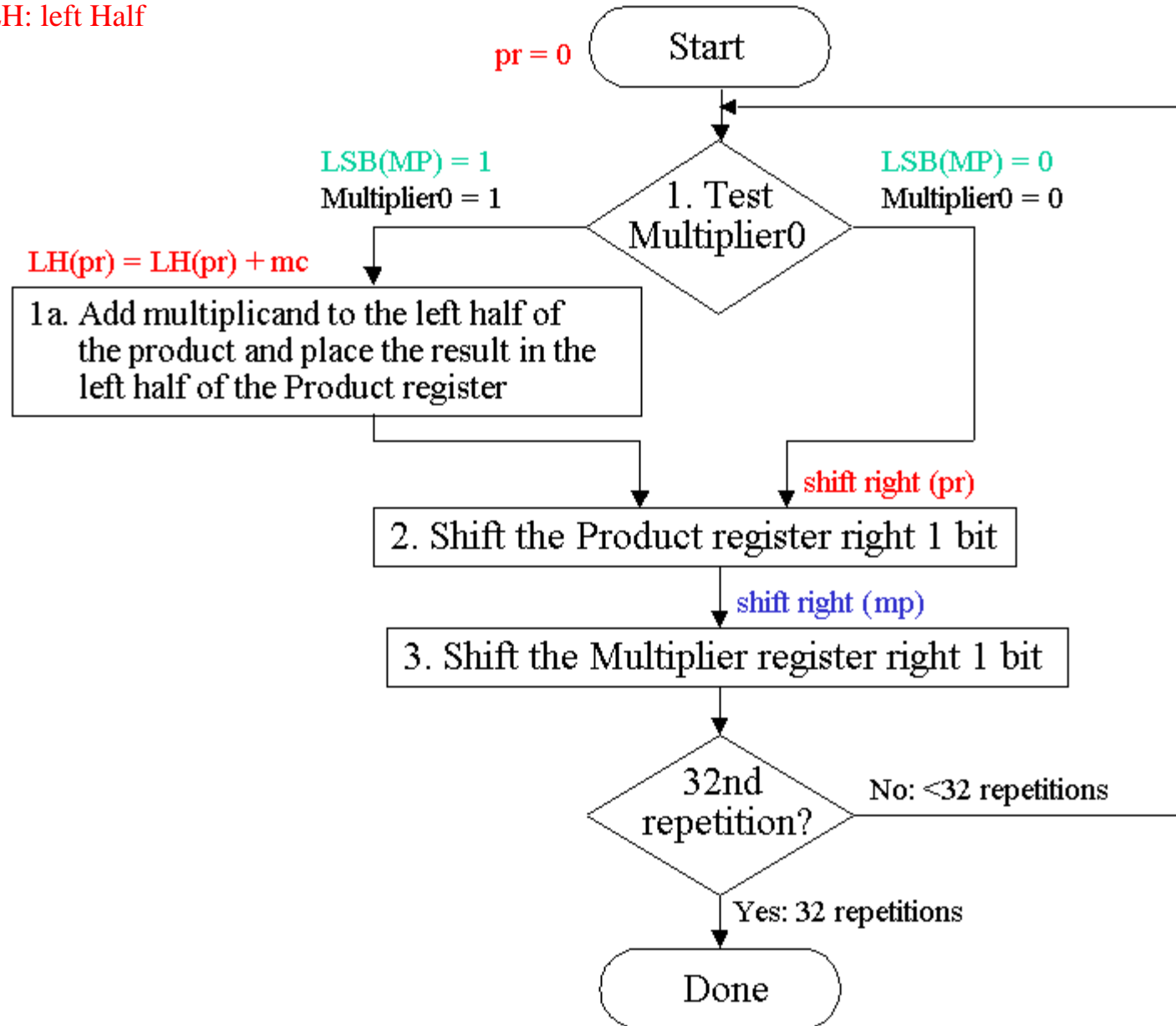

Multiply example using second algorithm


Iteration	Step	Multiplier	Multiplicand	Product
0	Initial Values	001 1	0010	0000 0000
1	1a: 1 => Prod=Prod+Mcand	0011	0010	0010 0000
	2: Shift right Product	0011	0010	0001 0000
	3: Shift right Multiplier	000 1	0010	0001 0000
2	1a: 1 => Prod=Prod+Mcand	0001	0010	0011 0000
	2: Shift right Product	0001	0010	0001 1000
	3: Shift right Multiplier	000 0	0010	0001 1000
3	1: 0 => no operation	0000	0010	0001 1000
	2: Shift right Product	0000	0010	0000 1100
	3: Shift right Multiplier	000 0	0010	0000 1100
4	1: 0 => no operation	0000	0010	0000 1100
	2: Shift right Product	0000	0010	0000 0110
	3: Shift right Multiplier	0000	0010	0000 0110

Multiplication hardware: third version

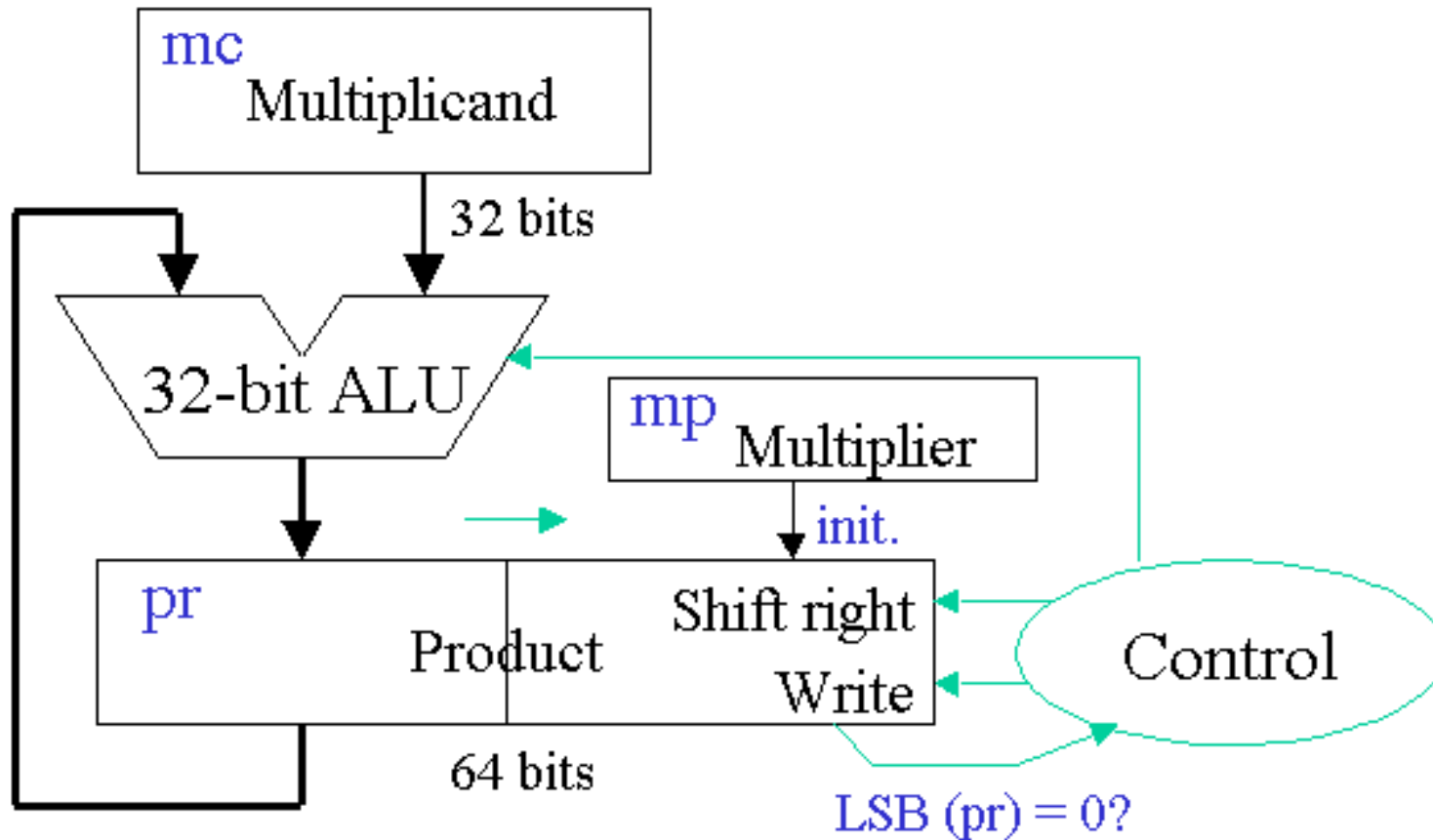

The separate Multiplier register disappeared. The multiplier is placed instead in the right half of the Product register.

$$pr = mp \times mc$$

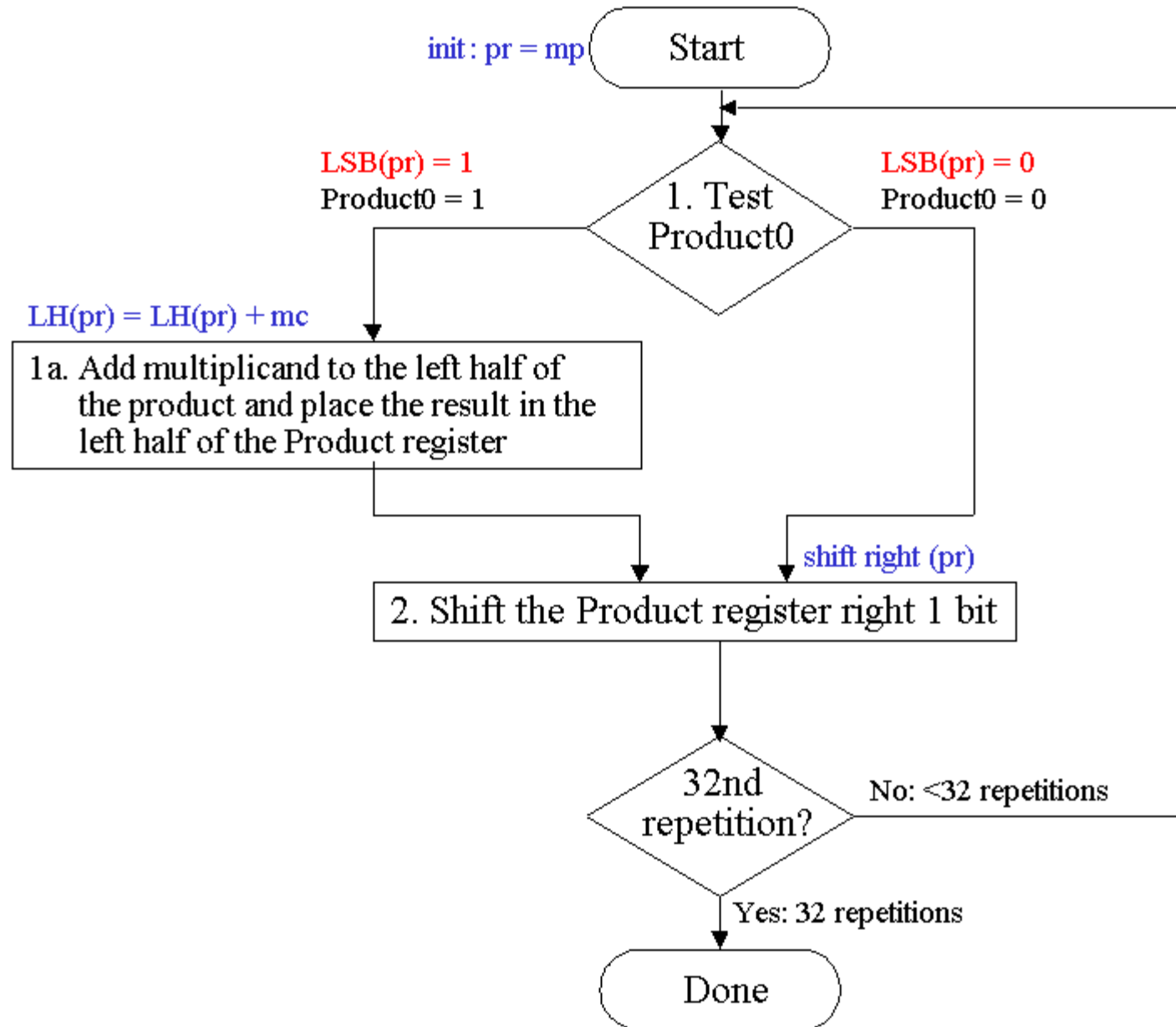

Multiply example using third algorithm

Iteration	Step	Multiplicand	Product
0	Initial Values	0010	0000 001 1
1	1a: 1 => Prod=Prod+Mcand 2: Shift right Product	0010 0010	0010 0011 0001 000 1
2	1a: 1 => Prod=Prod+Mcand 2: Shift right Product	0010 0010	0011 0001 0001 100 0
3	1: 0 => no operation 2: Shift right Product	0010 0010	0001 1000 0000 110 0
4	1: 0 => no operation 2: Shift right Product	0010 0010	0000 1100 0000 0110

Booth's insight

- substitute n additions by 1 subtraction, 1 addition
- successive 1s in multiplier **mp**
 \Rightarrow successive addition of shifted multiplicand **mc**

$$\begin{array}{rcl}
 & & 0010 \text{ mc} \\
 \times & & 0110 \text{ mp} \\
 \hline
 m = 00100 \xrightarrow{k=2} & & 0010 \text{ shift left mc since mp1} = 1 \\
 + & & 0010 \text{ shift left mc since mp2} = 1 \\
 \hline
 & & 001100
 \end{array}$$

- given number of 1s in $mp = k$, and initially shifted $mc = m$, then summing the k terms give:
 $m + 2m + 2^2m + \dots + 2^{k-1}m$ (geometric series)

Booth's algorithm

- replace summing k terms $m + 2m + \dots + 2^{k-1}m$ by 1 subtraction and 1 addition: $-m + 2^k m$ (and k shifts to get the 2^k factor)
- proof: let $S = 1 + 2 + \dots + 2^{k-1}$, so $2 \times S = 2 + 4 + \dots + 2^{k-1} + 2^k$
 $S = 2 \times S - S = 2^k + (2^{k-1} - 2^{k-1}) + \dots + (2 - 2) - 1 = 2^k - 1$
- exercise: check that it works for signed numbers
- algorithm detects a string of 1s in mp:

4 cases .. 0 1 1 1 1 .. 1 1 0 0 0

Comparing the third algorithm and Booth's algorithm for positive numbers

Iteration	Multi- plicand	Original algorithm		Booth's algorithm	
		Step	Product	Step	Product
0	0010	Initial Values	0000 0110	Initial Values	0000 0110 0
1	0010 0010	1: 0 => no operation 2: Shift right Product	0000 0110 0000 0011	1a: 00 => no operation 2: Shift right Product	0000 0110 0 0000 0011 0
2	0010 0010	1a: 1 => Prod=Prod+Mcand 2: Shift right Product	0010 0011 0001 0001	1c: 10 => Prod=Prod-Mcand 2: Shift right Product	1110 0011 0 1111 0001 1
3	0010 0010	1a: 1 => Prod=Prod+Mcand 2: Shift right Product	0011 0001 0001 1000	1d: 11 => no operation 2: Shift right Product	1111 0001 1 1111 0000 1
4	0010 0010	1: 0 => no operation 2: Shift right Product	0001 1000 0000 1100	1b: 01 => Prod=Prod+Mcand 2: Shift right Product	0001 1000 1 0000 1100 0

case {

- 00: middle of a string of 0s, no action
- 01: end of a string of 1s, pr = pr + shifted mc
- 10: start of a string of 1s, pr = pr - shifted mc
- 11: middle of a string of 1s, no action

then shift right pr

Division

- invented by Briggs
- Dividend = Quotient \times Divisor + Remainder


$$74 = 9 \times 8 + 2$$

- $$\begin{array}{r}
 \text{ds } 1000 \overline{) 1001010} \\
 \underline{-1000} \\
 0010 \\
 0101 \\
 1010 \\
 \underline{-1000} \\
 10
 \end{array}$$

q (r' : intermediate value)
align MSB(ds) and MSB(dd)
 $r' < ds: q = q ++ <0>$
 $r' \geq ds: q = q ++ <1>$
 10 r (r = r' when finished)


- compare r' and ds: calculate $r' = r' - ds$
 - $r' < 0$, $r' = r' + ds$ (restore old value of r')
 - $r' \geq 0$, accept r' for further calculation

First version of the division hardware

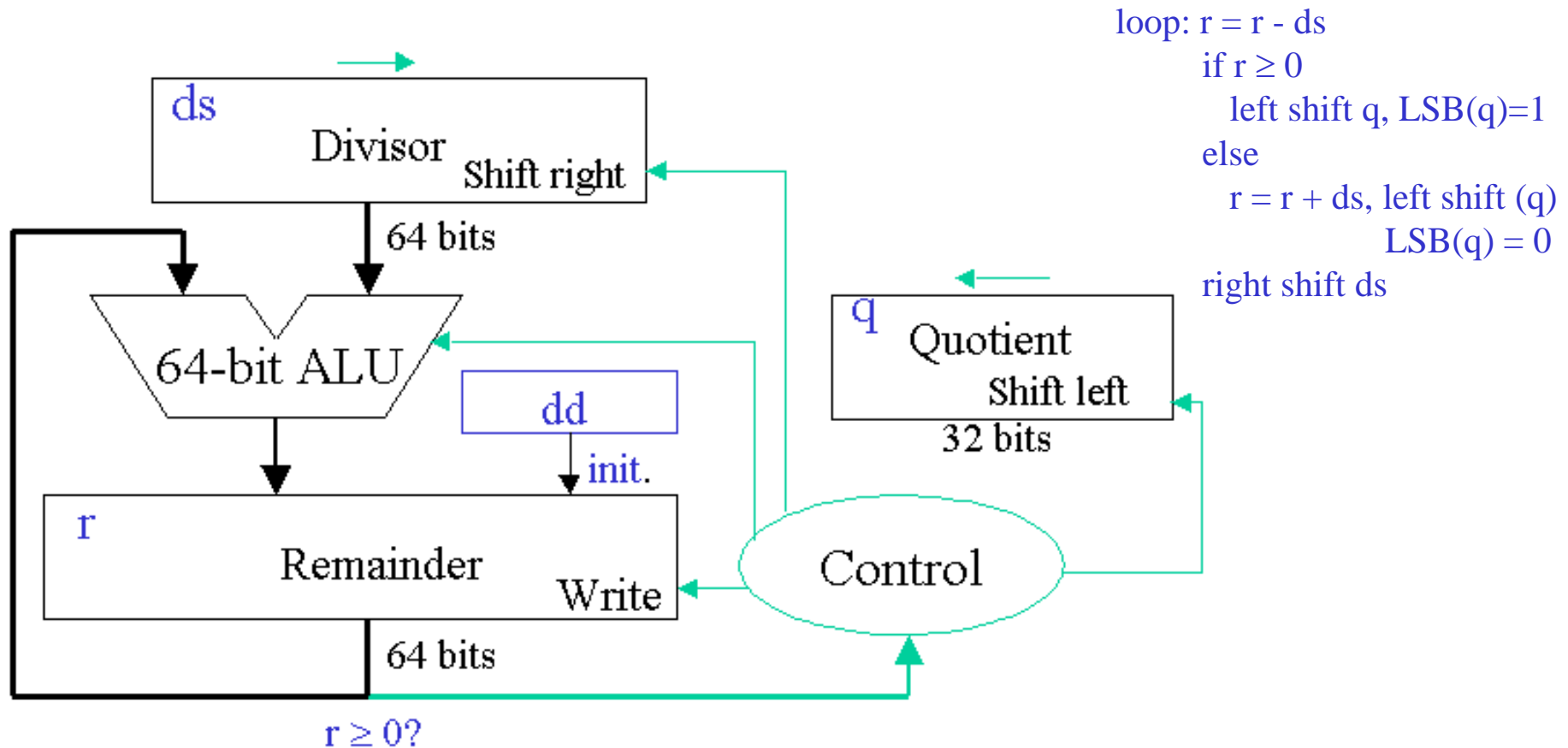

The Divisor register, ALU, and Remainder register are all 64 bits wide, with only the Quotient register being 32 bits. The 32-bit divisor starts in the left half of the Divisor register and is shifted right 1 bit on each step. The remainder is initialised with the dividend. Control decides when to shift the Divisor and Quotient registers and when to write the new value into the Remainder register.

$$dd = (q \times ds) + r$$

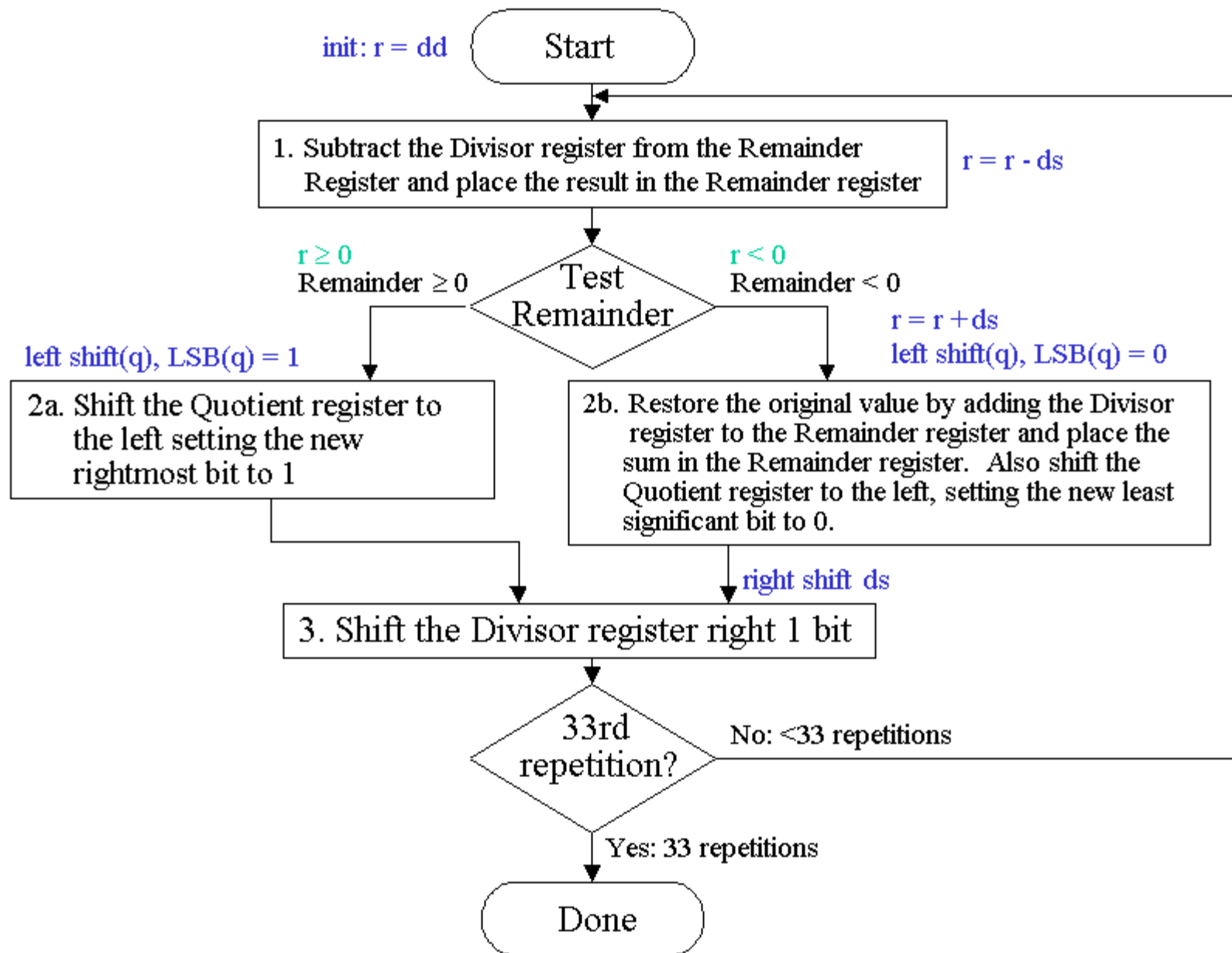

Division example using first algorithm

Iteration	Step	Quotient	Divisor	Remainder
0	Initial Values	0000	0010 0000	0000 0111
1	1: Rem = Rem - Div	0000	0010 0000	1 110 0111
	2b: Rem<0 \Rightarrow +Div, sll Q, Q0=0	0000	0010 0000	0000 0111
	3: Shift Div right	0000	0001 0000	0000 0111
2	1: Rem = Rem - Div	0000	0001 0000	1 111 0111
	2b: Rem<0 \Rightarrow +Div, sll Q, Q0=0	0000	0001 0000	0000 0111
	3: Shift Div right	0000	0000 1000	0000 0111
3	1: Rem = Rem - Div	0000	0000 1000	1 111 1111
	2b: Rem<0 \Rightarrow +Div, sll Q, Q0=0	0000	0000 1000	0000 0111
	3: Shift Div right	0000	0000 0100	0000 0111
4	1: Rem = Rem - Div	0000	0000 0100	0 000 0011
	2a: Rem \geq 0 \Rightarrow sll Q, Q0=1	0001	0000 0100	0000 0011
	3: Shift Div right	0001	0000 0010	0000 0011
5	1: Rem = Rem - Div	0001	0000 0010	0 000 0001
	2a: Rem \geq 0 \Rightarrow sll Q, Q0=1	0011	0000 0010	0000 0001
	3: Shift Div right	0011	0000 0001	0000 0001

dd=7 q=3
ds=2 r=1

To note

- refining division implementation
 - remainder shift left: reduce divisor / ALU size
 - combine quotient and remainder registers
- MIPS instructions
 - multu, divu: unsigned operations
 - result in HI, LO registers
 - mflo: move data from LO register
- exercise: signed numbers in
 - multiplication (3rd Ed: p.180, 4th Ed: p.234, 5th Ed: p.187)
 - division (3rd Ed: p.187, 4th Ed: p.239, 5th Ed: p.193)