

Computing without computers


(see notes on Hardware Compilation)

- computers are too slow, too bulky, consume too much power and energy
 - get rid of fetch/decode stage? ↓CPI? ↓clock delay?
- compile programs directly into hardware
 - hardware is parallel, hence fast
 - distributed control: no program counter
 - variables → registers, expressions → combinational circuit
 - applications: multimedia, communication, robotics
 - but hardware is inflexible?

Field-Programmable Gate Array (FPGA)

- a matrix of programmable elements, including: logic blocks, storage elements, interconnections
- 100K to 10000K gates: [system-on-a-chip](#), with [complex functions or instruction processors](#) e.g. ARM
- clock speed up to 800MHz (50-300MHz common)
- some can be reprogrammed within milliseconds ([even partially reprogrammable](#))
- off-the-shelf parts, see [altera.com](#), [xilinx.com](#), [maxeler.com](#)
[approaching speed of hardware,](#)
[flexibility of software](#)
- stand-alone or used with microprocessor
- 2015: Intel bought Altera, an FPGA company for US\$16.7B
- compilation method: basis for Handel-C tools
 - over 400 commercial seats, 600 academic seats

Stratix IVGX 230: mid-size FPGA

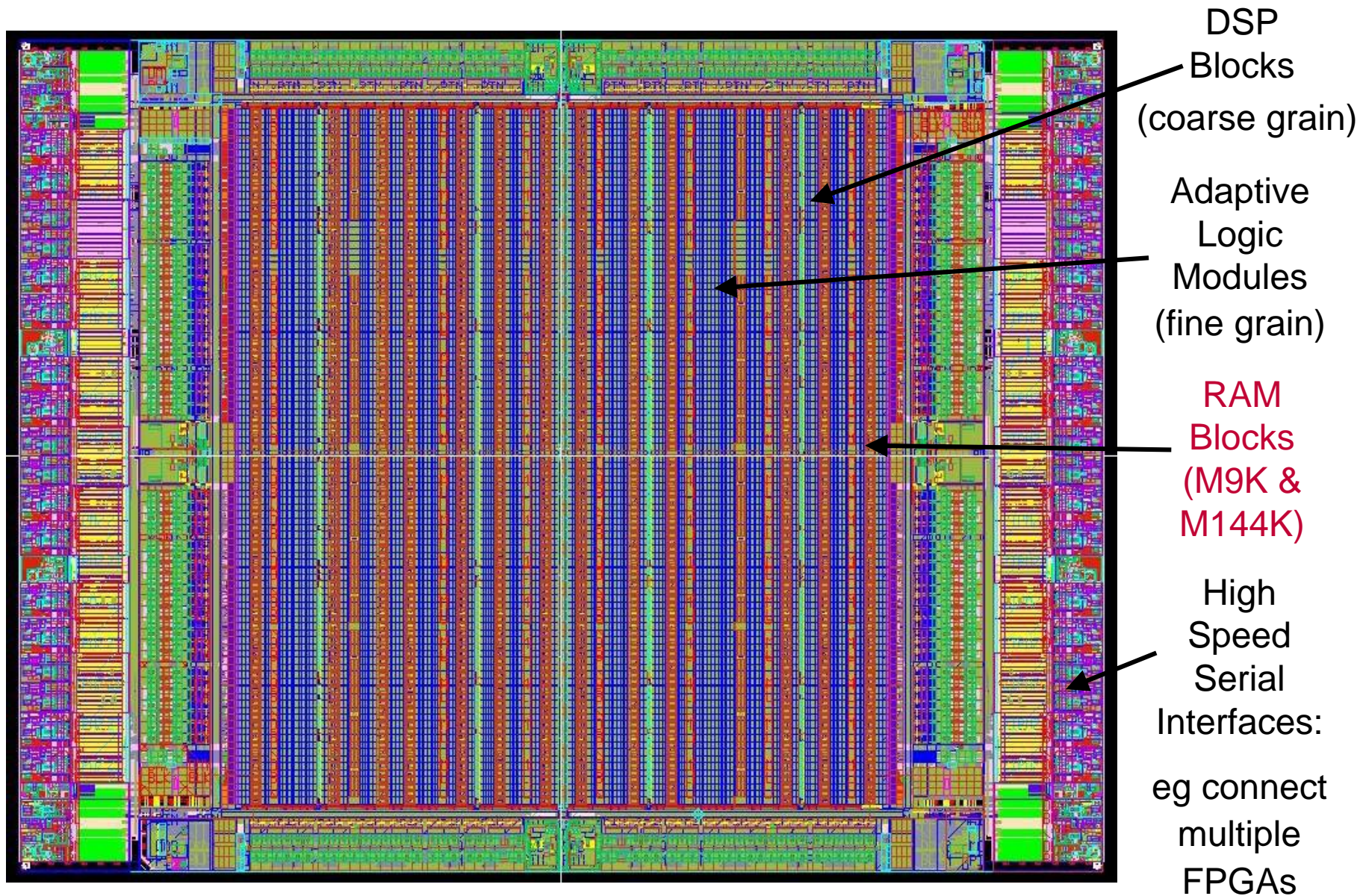

(source: V. Betz)

Occam and Handel-C

- based on CSP notation; commercial version: Handel-C
- primitive processes:

`skip` `stop` `v := e` `c ! e` `c ? e` `delay`

var → `v` `e` ← expr `c` ← chan output `c` ← chan input

- composite processes:

`SEQ P Q` `PAR P Q` `IF B P` `WHILE B P`
`ALT Bi Pi` (conditional on input ready in B_i)

- channel joins two processes at any time

one outputs
 the other inputs


$$\left[\begin{array}{l} \text{CHAN } C: \\ \text{PAR} \\ C ! E \\ C ? X \end{array} \right] = \left[\begin{array}{l} X := E \end{array} \right]$$

not examined

- produce data processors and instruction processors
- can also compile declarative programs into hardware

Expression and variable

 - expression: implemented using combinational hardware
 - no combinational loops
 - ensure propagation delay shorter than clock period (usually)
- variable: implemented using D type flip-flop and a multiplexor (mux)
 - mux allows conditional update of D type flip-flop (when $CE = 1$)




Control strategy

- use a single-cycle pulse (the token) to activate a control circuit (e.g. assignment)
- environment supplies a token to start (s), the token reappears at finish (f) when the statement completes execution
- control assumption: a control circuit does not create or destroy a token, provided that the environment does not offer a second token before the first token reappears
- the assignment circuit can accept token every cycle

Assignment statement $v := \text{exp}$

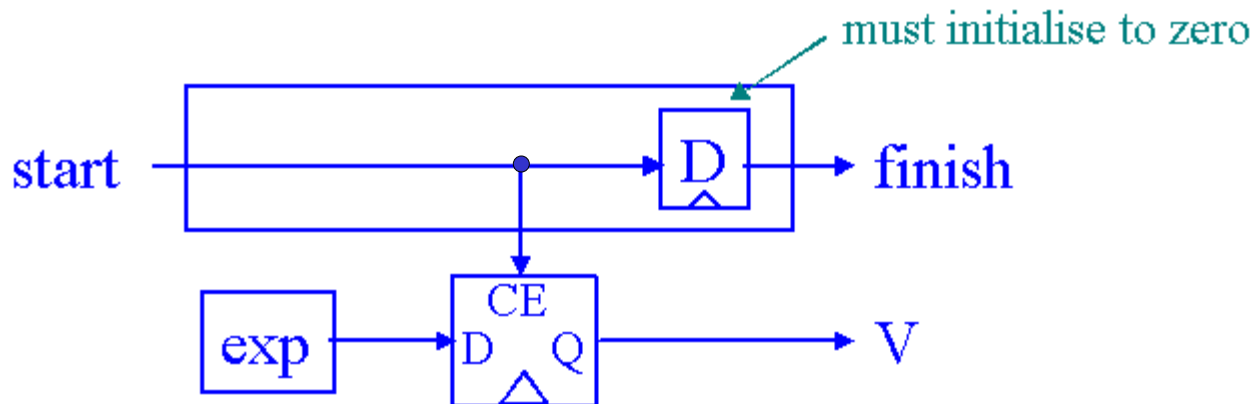
- provide control circuit to signal assignment, statement is completed after n cycles
- n depends on propagation delay of exp , usually $n=1$




- concurrent assignment: $v_0, v_1 := \text{exp}_0, \text{exp}_1$
use the same control circuit for the CE inputs
for v_0, v_1 hardware

Assignment: general case

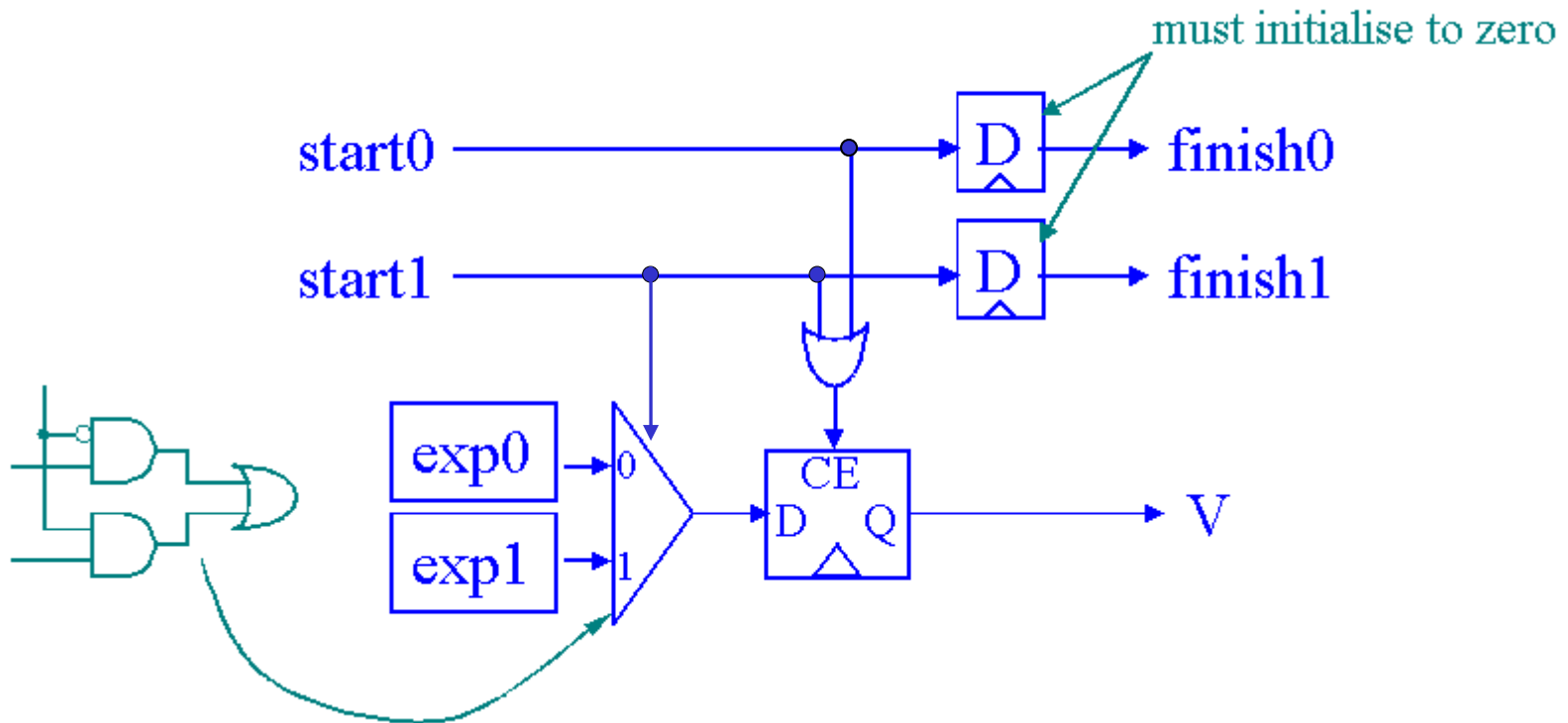- need multiplexing to support assigning different values to a variable at different times
e.g. $V := \text{exp0}; \dots ; V := \text{exp1}$





Initialisation

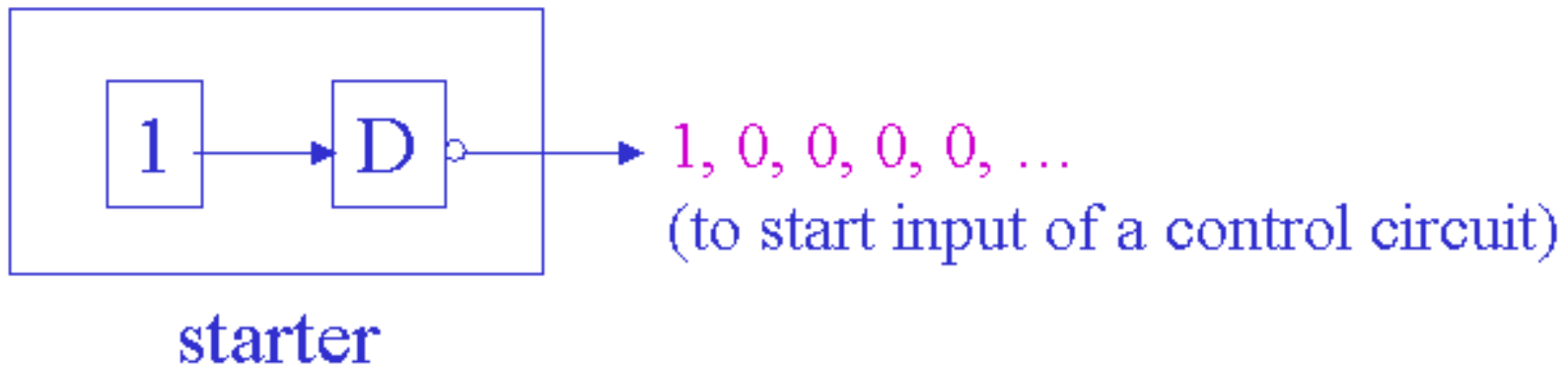

- provides the initial token to get system going
- assumes D-latch initialised to zero

Skip, delay and stop

  - skip: does nothing,
terminates immediately
- delay: does nothing,
terminates after 1 cycle
- stop: never terminates
perhaps raise an alarm




Sequential composition

SEQ
P
Q


or

P ; Q

 

- if P, Q satisfy the control assumption, then P;Q satisfies the control assumption
- only control signals are shown in the diagram


Conditional

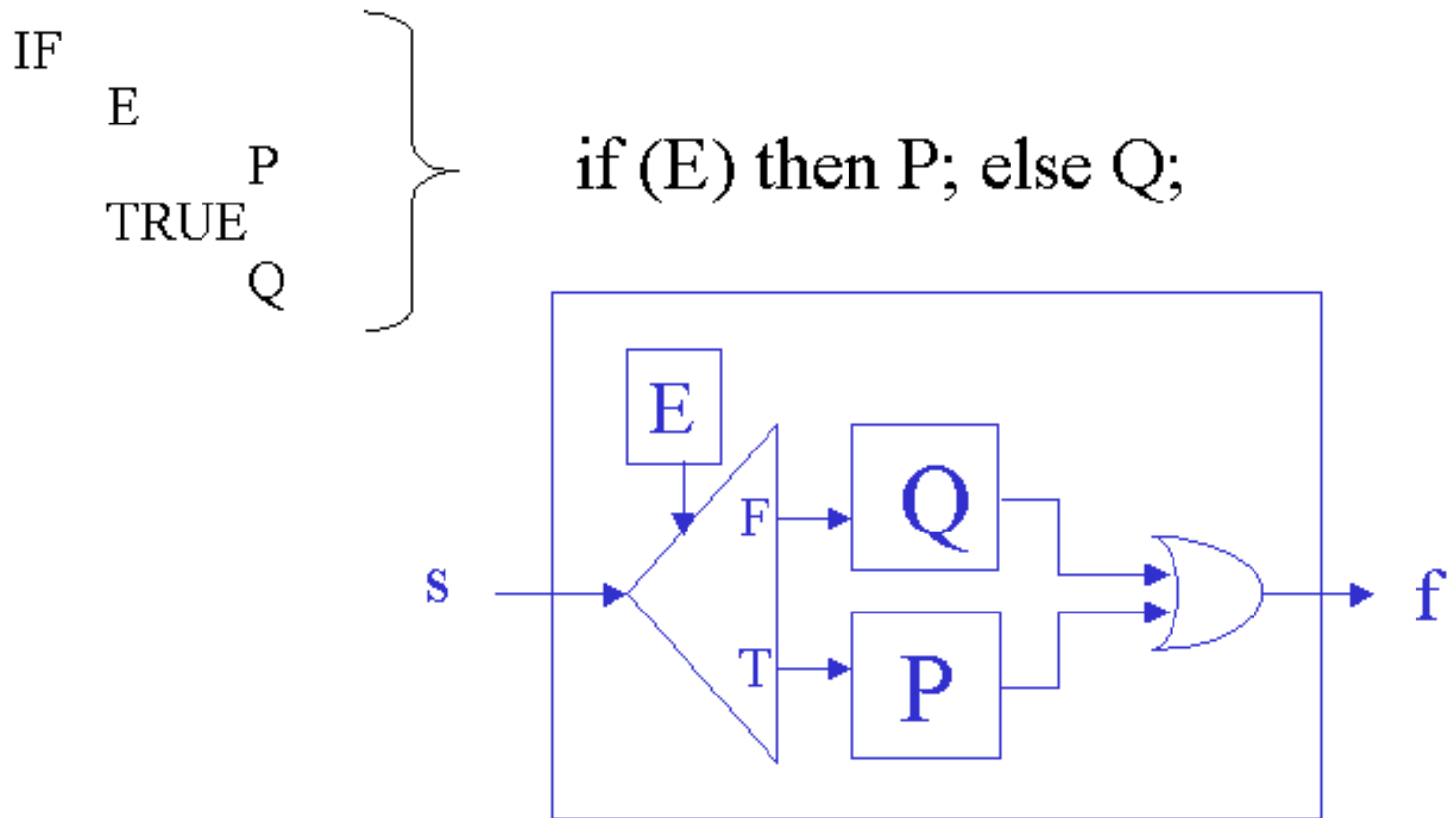

- either P or Q (not both)
should get the token


Iteration

WHILE E
 P or while (E) P

 

- what happens with the program
while (1) skip?


Example: simple data processor

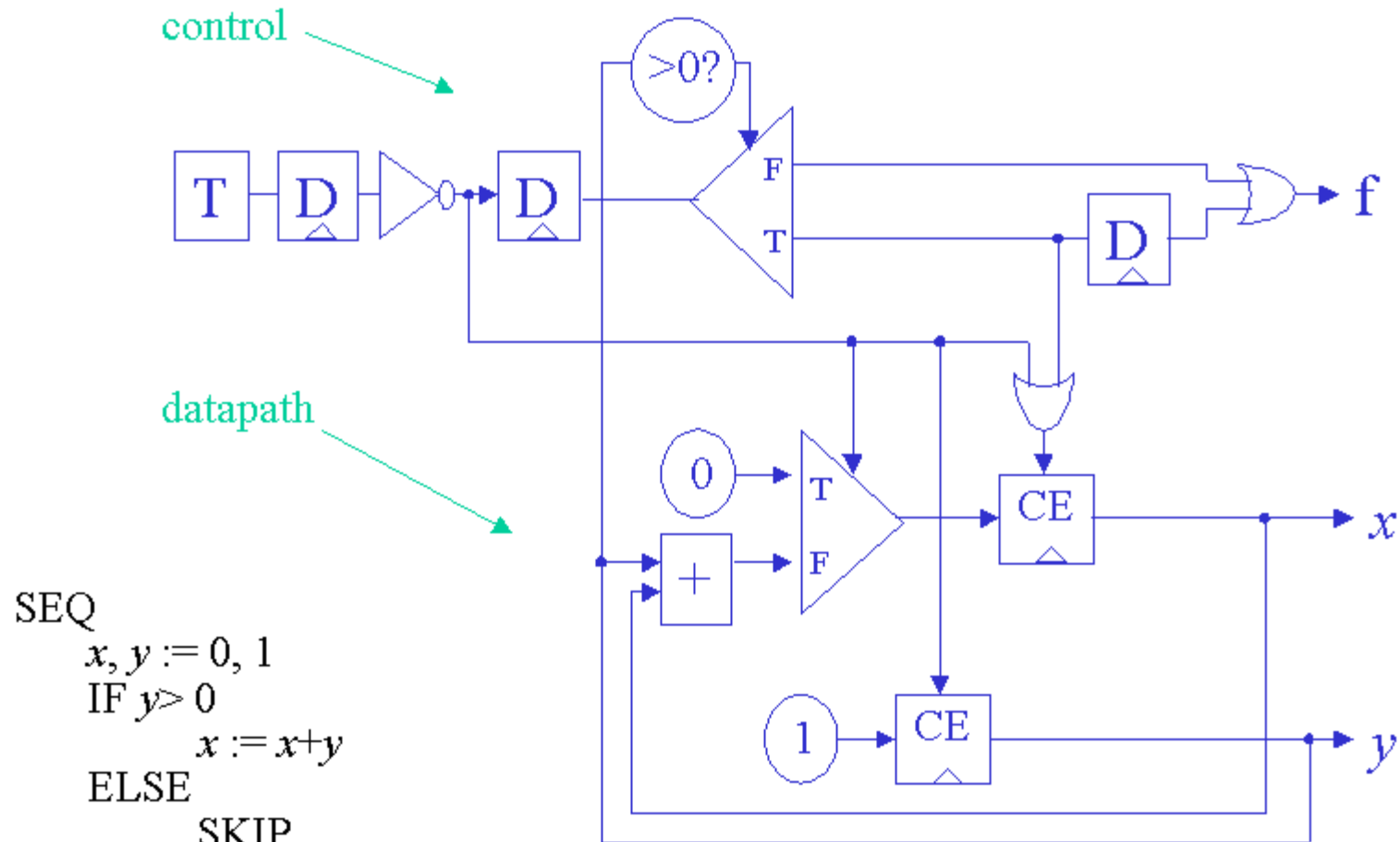

The par construct

- adding to parallelism in expression evaluation and concurrent assignment
- invokes program fragments in parallel, e.g.:
 - no variables in common, operating independently
 - communicate with each other via channels
 - share variables with each other, with restrictions
- terminates when all program fragments have terminated
- control circuit should have no time overhead:
 - start parallel execution immediately
 - terminate immediately when appropriate

Control circuit for par

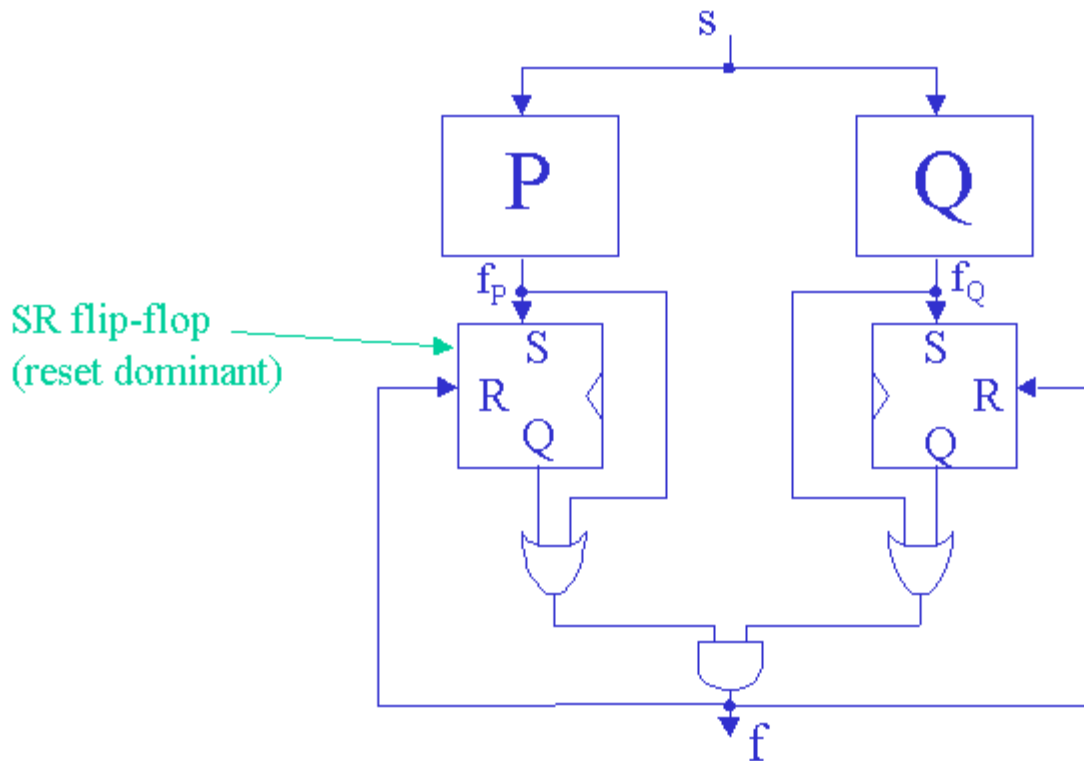

- PAR
 - P
 - Q
- or
- par { P;
 - Q

- SR flip-flop: once set, remains set until R input high
- or-gate: allows immediate termination