

IMPERIAL COLLEGE OF SCIENCE, TECHNOLOGY AND MEDICINE

EXAMINATIONS 2018

BEng Honours Degree in Computing Part I  
MEng Honours Degrees in Computing Part I  
for Internal Students of the Imperial College of Science, Technology and Medicine

*This paper is also taken for the relevant examinations for the  
Associateship of the City and Guilds of London Institute*

PAPER C112

HARDWARE

Friday 18th May 2018, 10:00

Duration: 80 minutes

*Answer ALL TWO questions*

Paper contains 2 questions  
Calculators not required

# 1 Four Mode Counter Circuit

A counter is to work in four modes determined by two input bits as follows.

- When the input is (0,0) the counter goes through the sequence 0,3,2,1,0,3,2,1, ...
- When the input is (0,1) the counter goes through the sequence 1,2,0,1,2,0, ...
- When the input is (1,0) the counter goes through the sequence 1,3,0,1,3,0, ...
- When the input is (1,1) the counter goes through the sequence 3,2,3,2, ...

- a
- i) Draw the state transition diagram that corresponds to the above specification.
  - ii) Construct a state transition table for the counter in the format given below. Use “don’t care” values wherever possible.

$I_1$	$I_0$	This State	$Q_1$	$Q_0$	Next State	$D_1$	$D_0$
0	0	0	0	0			
0	0	1	0	1			
0	0	2	1	0			
0	0	3	1	1			
0	1						
0	1						
0	1						
0	1						
1	0		etc				

- b Design the state sequencing logic that implements the above table. (You do not need to draw the circuit)
- c Given that the counter state is to be shown on a seven segment display, design the output logic that will provide the signal for the lower right vertical segment of the display.
- d Determine whether your circuit will work correctly for all possible changes of the inputs. There is no need to change your design if it could fail under certain conditions.


*The four parts carry equal marks.*

2a A 1-bit full subtractor circuit is defined by the following truth table:

<i>A</i>	<i>B</i>	<i>P</i>	<i>D</i>	<i>B</i>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Derive equations for *D* (the difference) and *B* (the borrow) starting from the canonical minterm form and simplifying them as far as possible.

 
- b Using a functional block of a 1-bit full subtractor (based on your design of the previous part) design a four bit subtractor circuit. Explain under what circumstances a “Payback-In” in would be required.
- c A 2-input 1-bit multiplexer is represented by the following functional block:




Design a circuit for this 2-input 1-bit multiplexer using only two input NAND gates.

- d Show how a 2-input NAND gate could be made using only two 2-input 1-bit multiplexers.

 - e The figure below shows two possible implementations for an enable circuit for an eight bit multiplexer. Which circuit will have the fastest response to a change in the input A? Explain your answer.



**Implementation 1**

 

**Implementation 2**

*The five parts carry equal marks.*