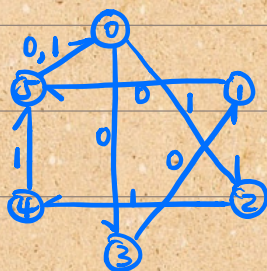


1a.



1b.

| Input | This State | Q2 | Q1 | Q0 | Next State | D2 | D1 | D0 |
|-------|------------|----|----|----|------------|----|----|----|
| 0     | 0          | 0  | 0  | 0  | 3          | 0  | 1  | 1  |
| 0     | 1          | 0  | 0  | 1  | 5          | 1  | 0  | 1  |
| 0     | 2          | 0  | 1  | 0  | X          | X  | X  | X  |
| 0     | 3          | 0  | 1  | 1  | 1          | 0  | 0  | 1  |
| 0     | 4          | 1  | 0  | 0  | X          | X  | X  | X  |
| 0     | 5          | 1  | 0  | 1  | 0          | 0  | 0  | 0  |
| 0     | X          | 1  | 1  | 0  | X          | X  | X  | X  |
| 0     | X          | 1  | 1  | 1  | X          | X  | X  | X  |
| 1     | 0          | 0  | 0  | 0  | 2          | 0  | 1  | 0  |
| 1     | 1          | 0  | 0  | 1  | X          | X  | X  | X  |
| 1     | 2          | 0  | 1  | 0  | 4          | 1  | 0  | 0  |
| 1     | 3          | 0  | 1  | 1  | X          | X  | X  | X  |
| 1     | 4          | 1  | 0  | 0  | 5          | 1  | 0  | 1  |
| 1     | 5          | 1  | 0  | 1  | 0          | 0  | 0  | 0  |
| 1     | X          | 1  | 1  | 0  | X          | X  | X  | X  |
| 1     | X          | 1  | 1  | 1  | X          | X  | X  | X  |

1c. K-map for  $D_2$ :

| Q <sub>2</sub> Q <sub>0</sub> | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00                            | 0  | 1  | 0  | X  |
| 01                            | X  | 0  | X  | X  |
| 11                            | 1  | 0  | X  | X  |
| 10                            | 0  | X  | X  | 1  |

$$D_2 = Q_2 \cdot Q_1' \cdot Q_0' + Q_2' \cdot Q_1' \cdot Q_0 + I \cdot Q_1$$

K-map for  $D_1$ :

| Q <sub>2</sub> Q <sub>0</sub> | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00                            | 1  | 0  | 0  | X  |
| 01                            | X  | 0  | X  | X  |
| 11                            | 0  | 0  | X  | X  |
| 10                            | 0  | X  | X  | 0  |


K-map for  $D_0$ :

| Q <sub>2</sub> Q <sub>0</sub> | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00                            | 1  | 1  | 1  | X  |
| 01                            | X  | 0  | X  | X  |
| 11                            | 1  | 0  | X  | X  |
| 10                            | 0  | X  | X  | 0  |

$$D_1 = Q_2' \cdot Q_1' \cdot Q_0'$$

$$D_0 = I' \cdot Q_2' + Q_2 \cdot Q_0'$$

1d.

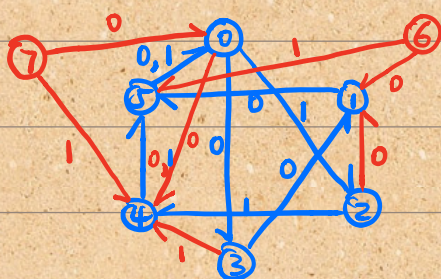

For all possible unexpected state, it will finally be back on the right track.

1e. K-map for  $D_1$ :

| Q <sub>2</sub> Q <sub>0</sub> | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 0                             | 0  | 1  | 1  | 0  |
| 1                             | 0  | 1  | 1  | 0  |

$$D_1 = Q_0$$

K-map for  $D_2$ :

| Q <sub>2</sub> Q <sub>0</sub> | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 0                             | 1  | 0  | 0  | 1  |
| 1                             | 1  | 0  | 0  | 1  |

$$D_2 = Q_0'$$

Circuit (Not part of the question):






2a. K-map for output

|          |          |    |    |    |
|----------|----------|----|----|----|
|          | $b_1b_0$ |    |    |    |
| $b_3b_2$ | 00       | 01 | 11 | 10 |
| 00       | 0        | 0  | 0  | 0  |
| 01       | 0        | 0  | 0  | 0  |
| 11       | 1        | 1  | 1  | 1  |
| 10       | 0        | 0  | 1  | 1  |

$$\text{Output} = b_3 \cdot b_2 + b_3 \cdot b_1 = b_3 \cdot (b_2 + b_1)$$

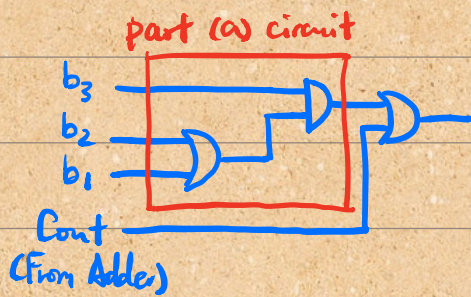b. Any sum bigger than 9 should be considered here:


if the sum becomes an invalid combination, there should be a carry-out:




c. Decimal 10 11 12 The 4-bit number should be 0110<sub>binary</sub>

Binary 1010 1011 1100

BCD 0000 0001 0010

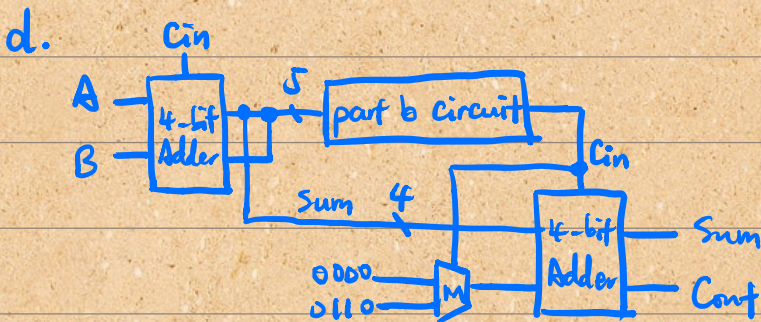

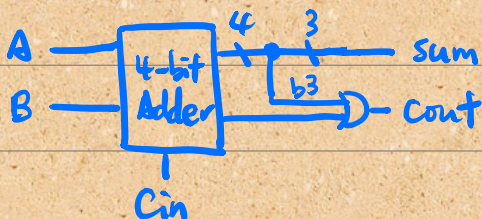e. Any bigger than 7 should incur a carry to the next digit



(Assuming A and B are both within the range 0-7)