

IMPERIAL COLLEGE OF SCIENCE, TECHNOLOGY AND MEDICINE

EXAMINATIONS 2019

BEng Honours Degree in Computing Part I
MEng Honours Degrees in Computing Part I
for Internal Students of the Imperial College of Science, Technology and Medicine

*This paper is also taken for the relevant examinations for the
Associateship of the City and Guilds of London Institute*

PAPER C112

HARDWARE

Friday 17th May 2019, 14:00
Duration: 80 minutes


Answer ALL TWO questions

Paper contains 2 questions
Calculators not required


Section A (Use a separate answer book for this Section)

1 Functional Design and Computer Arithmetic

 - a Using only four 2-input NAND gates and two 2-input NOR gates, design a circuit for a 2-input one bit multiplexer with an “enable” input. If the enable input is at logic 1, the circuit behaves as a normal multiplexer, if it is at logic 0, the circuit output is zero.




 - b Using only two of the multiplexer circuits of part a, two 2-input NAND gates, and two 2-input NOR gates, design a four input one-bit multiplexer with an enable input.



- c A half subtractor is defined by the following Boolean equations and circuit:
 
$$\begin{aligned} \text{Difference} &= A \oplus B \\ \text{Borrow} &= \bar{A} \cdot B \end{aligned}$$



- i) Show how two half subtractors and one OR gate can be connected to make a full subtractor which includes a payback input (C_{in}).
 - ii) Show how two full subtractors can be connected up to make a two-bit full subtractor with a carry input (C_{in}) and a carry output (C_{out}). The carry input is provided to allow high precision integer arithmetic to be performed.
- d As an alternative to the above approach, design a two-bit two's complement subtractor, with a carry input and a carry output, using two full adders and some NAND gates. Each full adder is thereby defined as follows, where C_{in} is the carry input, and C_{out} is the carry output:
- $$\begin{aligned} \text{Sum} &= A \oplus B \oplus C_{in} \\ \text{Cout} &= C_{in} \cdot (A \oplus B) + A \cdot B \end{aligned}$$
- e Design a simple two bit ALU circuit which has a single one-bit function select input F , two two-bit inputs A and B , and a one-bit carry output (C_{out}). If $F = 0$, the output of the ALU is $A - B$; if $F = 1$, the output of the ALU is $A + B$. You can use the circuits in parts c and d, a two-way two-input multiplexer, and a single-way two-input multiplexer as functional blocks in your circuit.

The five parts carry equal marks.

Section B (Use a separate answer book for this Section)


2 Combinational Circuit Design and feedback

- a Using Boolean algebra, simplify the following Boolean expression to its simplest form (fewest number of literals):

$$E = A' \cdot B' \cdot (A' + B) \cdot (B' + B),$$

where \cdot , $+$, and $'$ represent “AND”, “OR” and “NOT” operations respectively. Please show the sequence of your steps and state the reduction rules used explicitly.

- b
- Draw the schematic logic circuit for a basic SR-Latch 1-bit memory unit.
 - Briefly describe what your circuit does and derive its truth table.
 - What is the difference between synchronous and asynchronous logic circuits?
 - Is the 1-bit SR-Latch a synchronous or asynchronous logic circuit?
 - If the input (R,S) to your circuit of part b(i) changes from (1,0) to (1,1) explain what will happen to the output.
 - If the input to your circuit of part b(i) changes from (0,0) to (1,1) explain what will happen to the output.
- c The J-K flip flop, commonly used in hardware design, is a circuit with two inputs labelled J and K, and complementary Q and Q' outputs. It is defined by the following finite state machine, where the inputs are shown as tuples (J,K).

 

- From the finite state machine construct the state transition table of the J-K flip-flop.
 - Design a circuit for the J-K flip flop using one D-Type flip-flop and whatever other gates you require.
- d Explain briefly how spikes can occur in combinational logic circuit outputs.

The four parts carry, respectively, 20%, 30%, 40%, and 10% of the marks.