
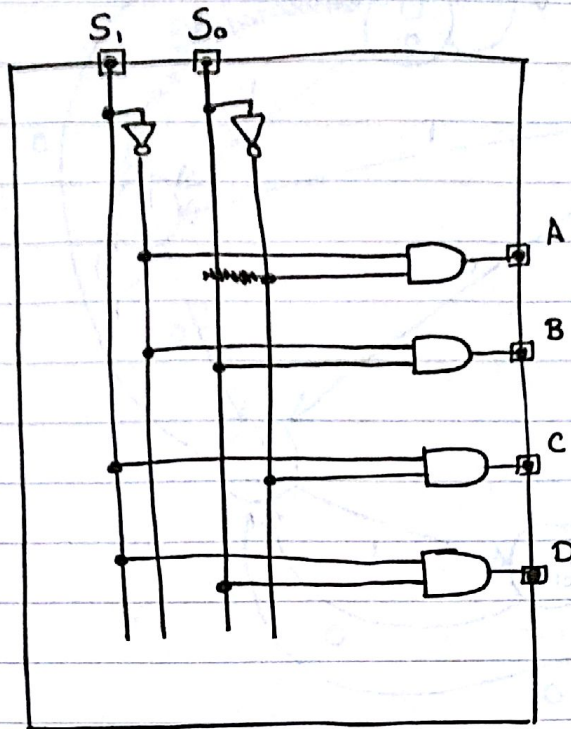


2013


1) a)

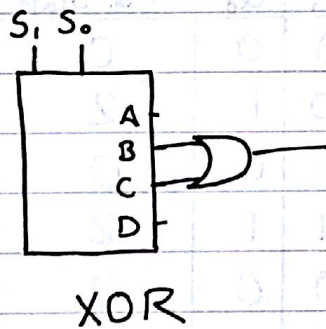

b) i)



ii)

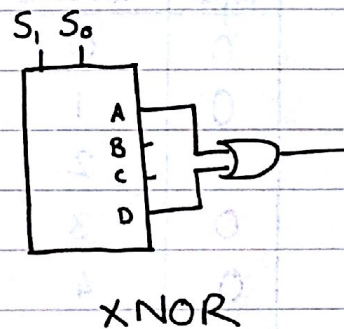

c)

A	B	G	E
0	0	0	1
0	1	0	0
1	0	1	0
1	1	0	1


$$\begin{aligned}
 G &= A \cdot B' \\
 &= (A' + B)' \\
 &= ((A + A)' + B)'
 \end{aligned}$$

$$\begin{aligned}
 E &= A' \cdot B' + A \cdot B \\
 &= (A + B)' + (A' + B')' \\
 &= (((A + B)' + ((A + A)' + (B + B)'))')'
 \end{aligned}$$





2) a)

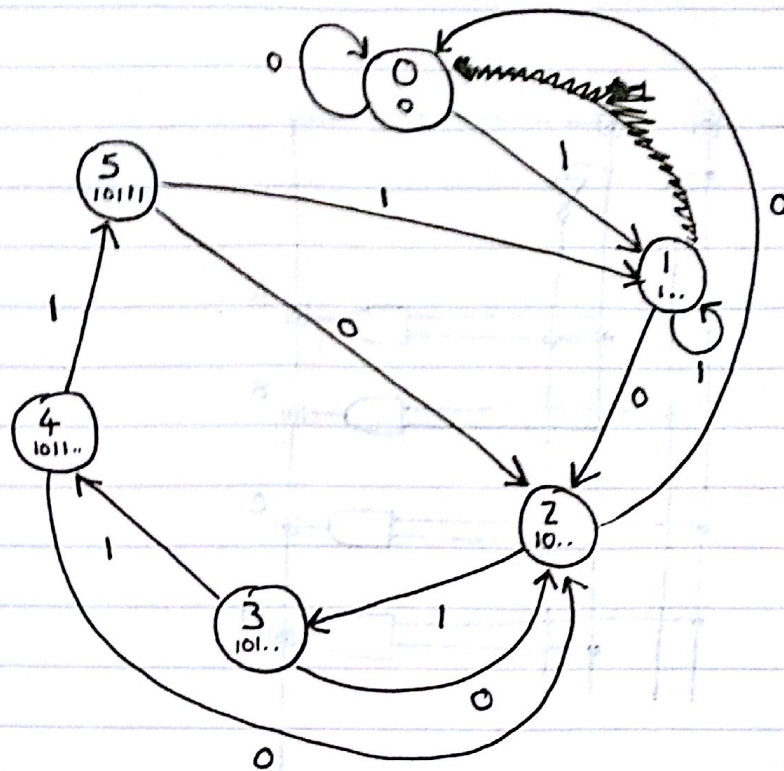

b)

Input	This State	$Q_2$	$Q_1$	$Q_0$	Next State	D2	D1	D0
0	0	0	0	0	0	0	0	0
0	1	0	0	1	2	0	1	0
0	2	0	1	0	0	0	0	0
0	3	0	1	1	2	0	1	0
0	4	1	0	0	2	0	1	0
0	5	1	0	1	2	0	1	0
0		1	1	0	X	X	X	X
0		1	1	1	X	X	X	X
1	0	0	0	0	1	0	0	1
1	1	0	0	1	1	0	0	1
1	2	0	1	0	3	0	1	1
1	3	0	1	1	4	1	0	0
1	4	1	0	0	5	1	0	1
1	5	1	0	1	1	0	0	1
1		1	1	0	X	X	X	X
1		1	1	1	X	X	X	X

D2

		Q <sub>1</sub> Q <sub>0</sub>			
		00	01	11	10
IQ <sub>2</sub>	00	0	0	0	0
	01	0	0	X	X
	11	1	0	X	X
	10	0	0	1	0

D1

		Q <sub>1</sub> Q <sub>0</sub>			
		00	01	11	10
IQ <sub>2</sub>	00	0	1	1	0
	01	1	1	X	X
	11	0	0	X	X
	10	0	0	0	1

D0

		Q <sub>1</sub> Q <sub>0</sub>			
		00	01	11	10
IQ <sub>2</sub>	00	0	0	0	0
	01	0	0	X	X
	11	1	1	X	X
	10	1	1	0	1

$$D2 = I \cdot Q_2 \cdot Q_0' + I \cdot Q_1 \cdot Q_0$$

$$D1 = I' \cdot Q_2 + I' \cdot Q_0 + I \cdot Q_1 \cdot Q_0'$$

$$D0 = I \cdot Q_1' + I \cdot Q_0'$$

d.)

Input	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Next State	D2	D1	D0
0	1	1	0	2	0	1	0
0	1	1	1	0	0	0	0
1	1	1	0	7	1	1	1
1	1	1	1	4	1	0	0

If the circuit starts in one of the unassigned states, it will fall into one of the known states straight away. The circuit will, however, think it is part way through the sequence unless some kind of reset is added.



$$e) \quad 0 \equiv Q_2 \cdot Q'_1 \cdot Q_0$$